 


# Lab #6

## Lab Report

---




### Introduction

The purpose of this lab is to simulate and experimentally characterize inverters based on integrated circuit PMOS and NMOS devices. We find that there are differences between transistors we design with these and discrete MOS components. These integrated circuit models, once tested, can be used to expand on CMOS digital logic design. If speed is considered, different design techniques should be considered to handle increased fan-in.


# Results

## 1 CMOS Inverter Voltage Transfer Characteristics

### Part 1.1 Inverter Circuit

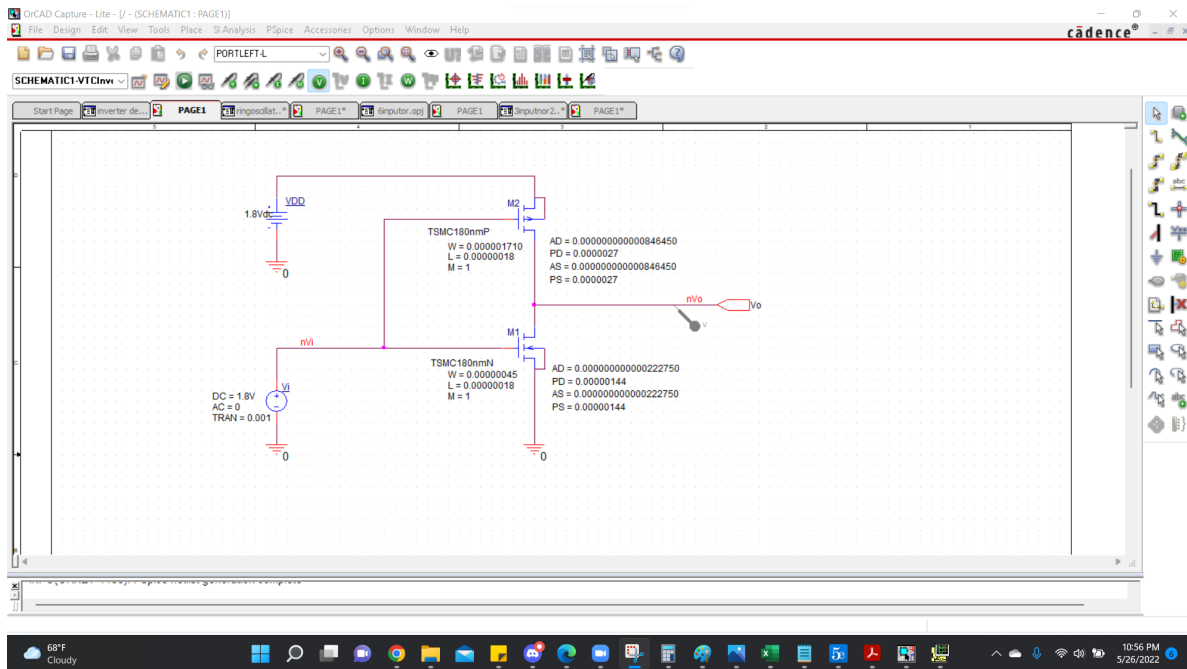

**Figure 1.1.1** Screen capture of the schematic, and the date and time.

 

**Figure 1.1.2** Simulation VTC

 


Figure 1.1.3 Measuring  $V_M$

 


Figure 1.1.4 Measuring  $V_{IL}$

 


Figure 1.1.5 Measuring  $V_{IH}$

 


Figure 1.1.6 Measuring  $V_{OH}$


 


Figure 1.1.7 Measuring  $V_{OL}$

 

Figure 1.1.8 Measuring power function



**Figure 1.1.9** Measuring Peak Power

Parameter	Value
$V_M$	0.900 V
$V_{OH}$	1.800 V
$V_{OL}$	0.000 V
$V_{IH}$	1.014 V
$V_{IL}$	0.780 V
$NM_H$	0.786 V
$NM_L$	0.780 V
$P_{peak}$	0.104 mW

**Table 1.1.1** Simulation measurements



## 2 Ring Oscillator

### Part 2.1 Ring Oscillator Circuit

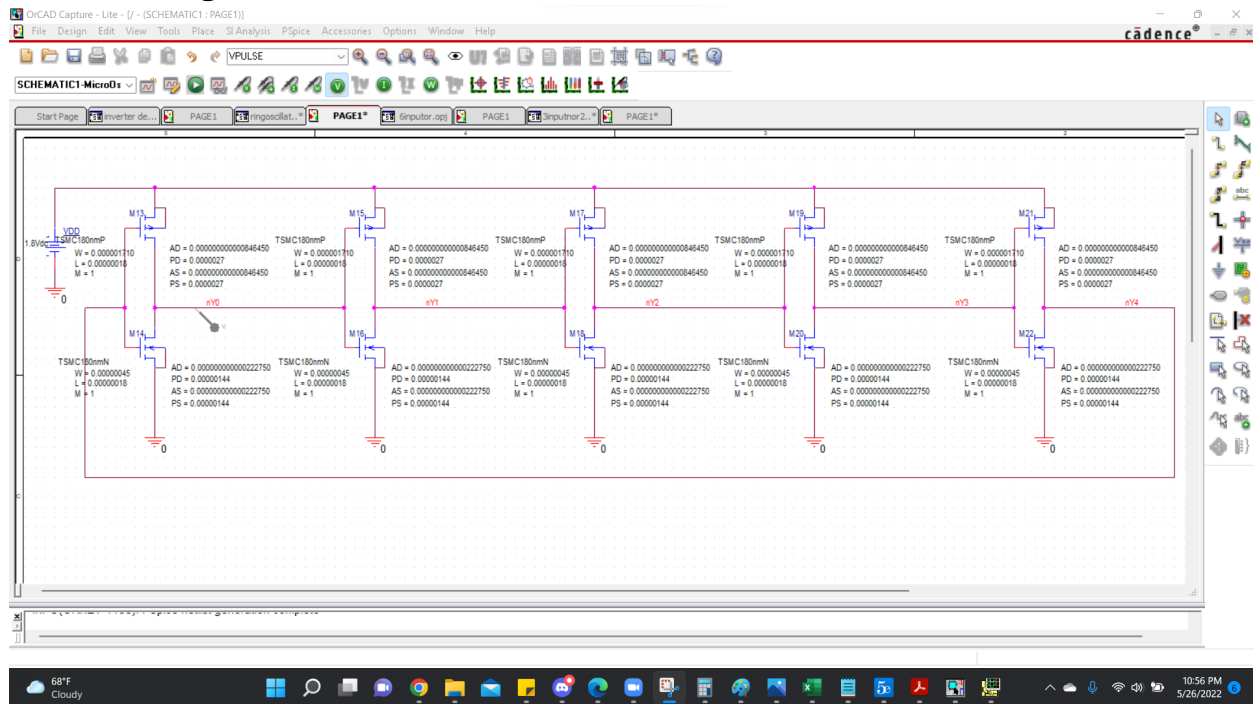


Figure 2.1.1 Ring Oscillator Circuit

### Part 2.2 Ring Oscillator Circuit Simulation


 


Figure 2.2.1 Ring Oscillator working

 

**Figure 2.2.2** Measure  $t_r$ ,  $t_f$ ,  $t_{PHL}$ ,  $t_{PLH}$ , and  $T$ .

Parameter	Value
$t_r$ ( $t_{TLH}$ )	52.31ps
$t_f$ ( $t_{THL}$ )	58.79ps
$t_{PHL}$	49.69ps
$t_{PLH}$	44.32ps
$t_p$	47.00ps
$T$	445ps

**Table 2.2.1** Simulation measurements



## Part 2.3 Ring Oscillator Circuit Experimentation



**Figure 2.3.1** Measurement of real circuit signals

Parameter	Simulated Values	Experimental Values
$t_r$ ( $t_{TLH}$ )	52.31ps	1.321us
$t_f$ ( $t_{THL}$ )	58.79ps	1.137us
$t_{PHL}$	49.69ps	772.743ns
$t_{PLH}$	44.32ps	1.137us
$t_p$	47.00ps	0.945 us
$T$	445ps	7.051us

**Table 2.3.1** Measurements comparison.

# 3 Ring Oscillator

## Part 3.1 6 input OR Circuit

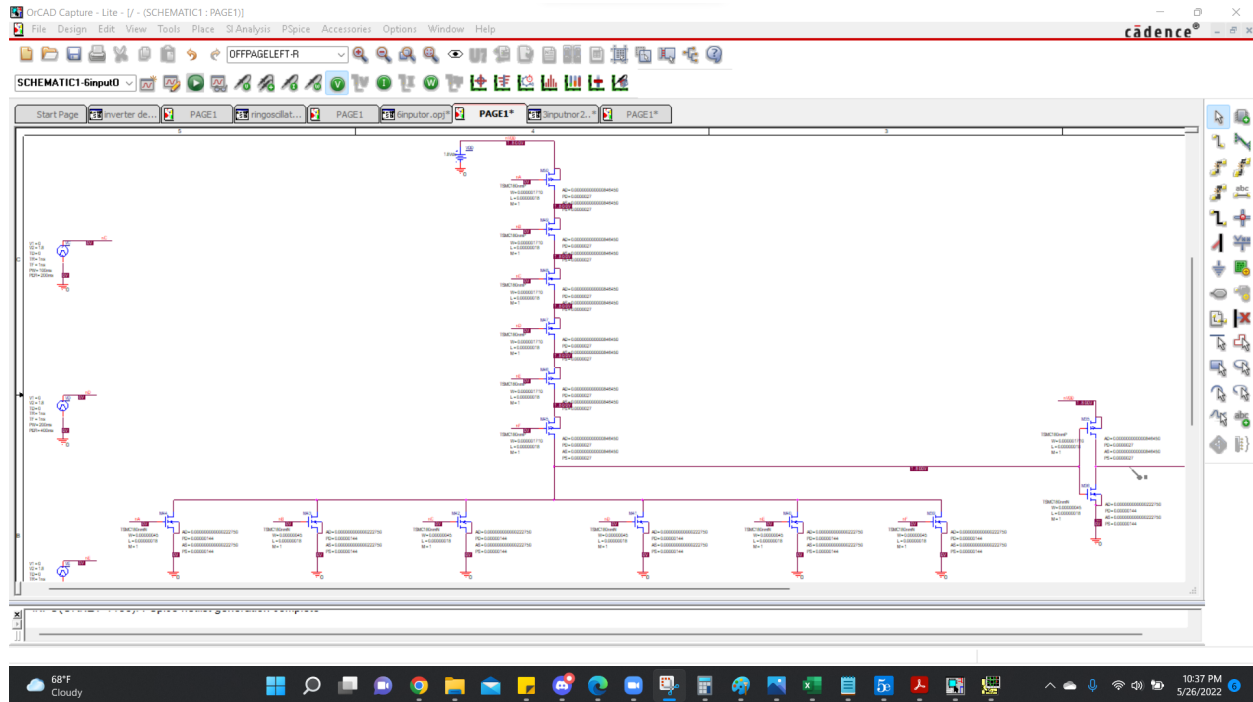


Figure 3.1.1 6 input OR circuit schematic



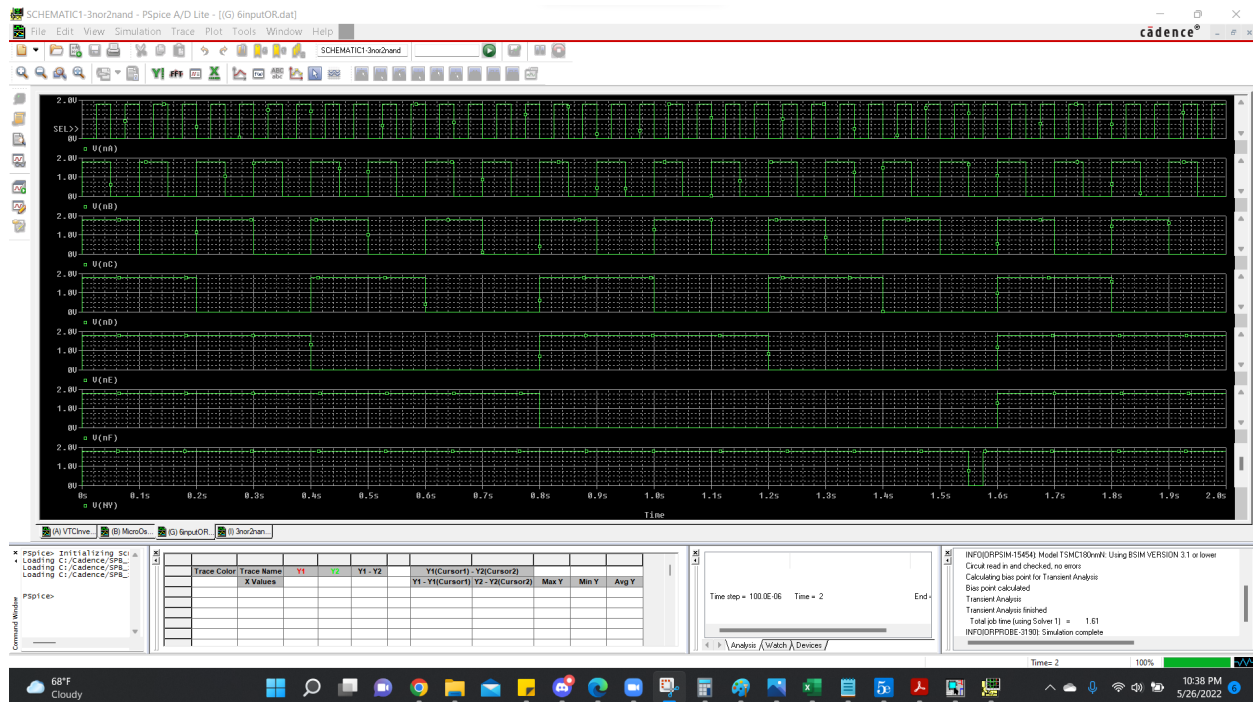



Figure 3.1.2 6 input OR circuit results

 


**Figure 3.1.3** 6 input OR circuit simulation to measure delays.

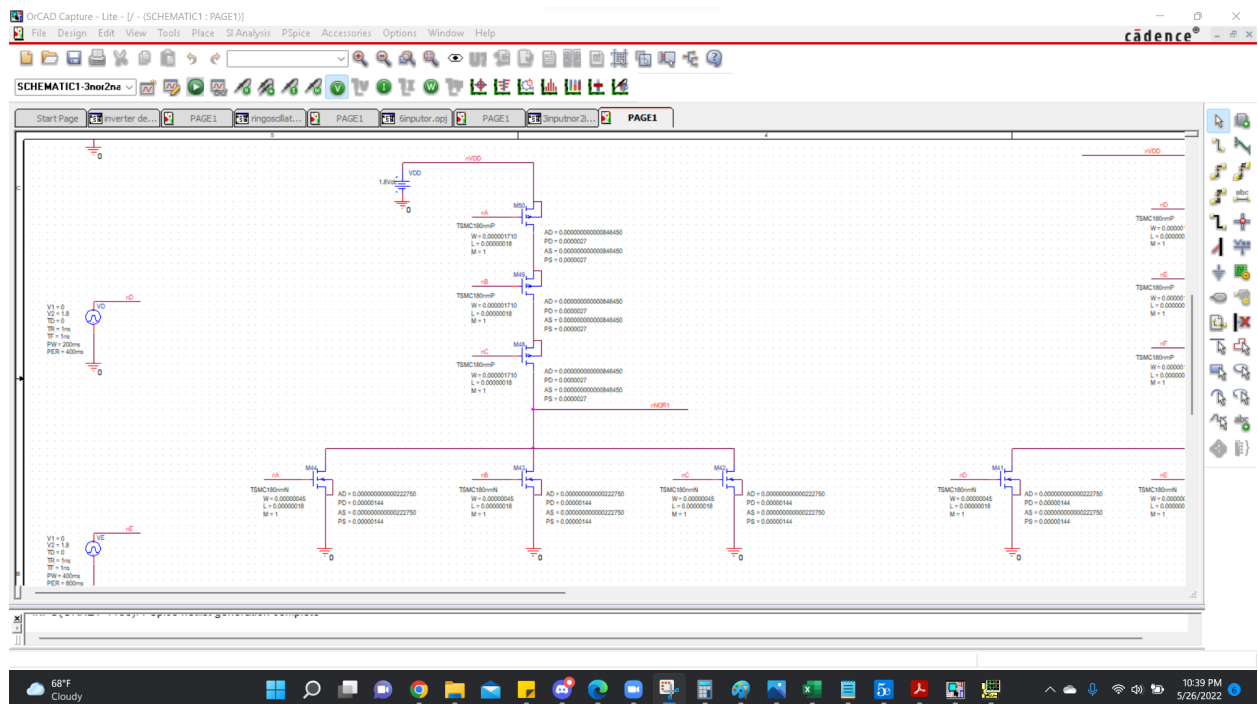


**Figure 3.1.4** 3 input NOR circuit schematic for 6 input OR implementation

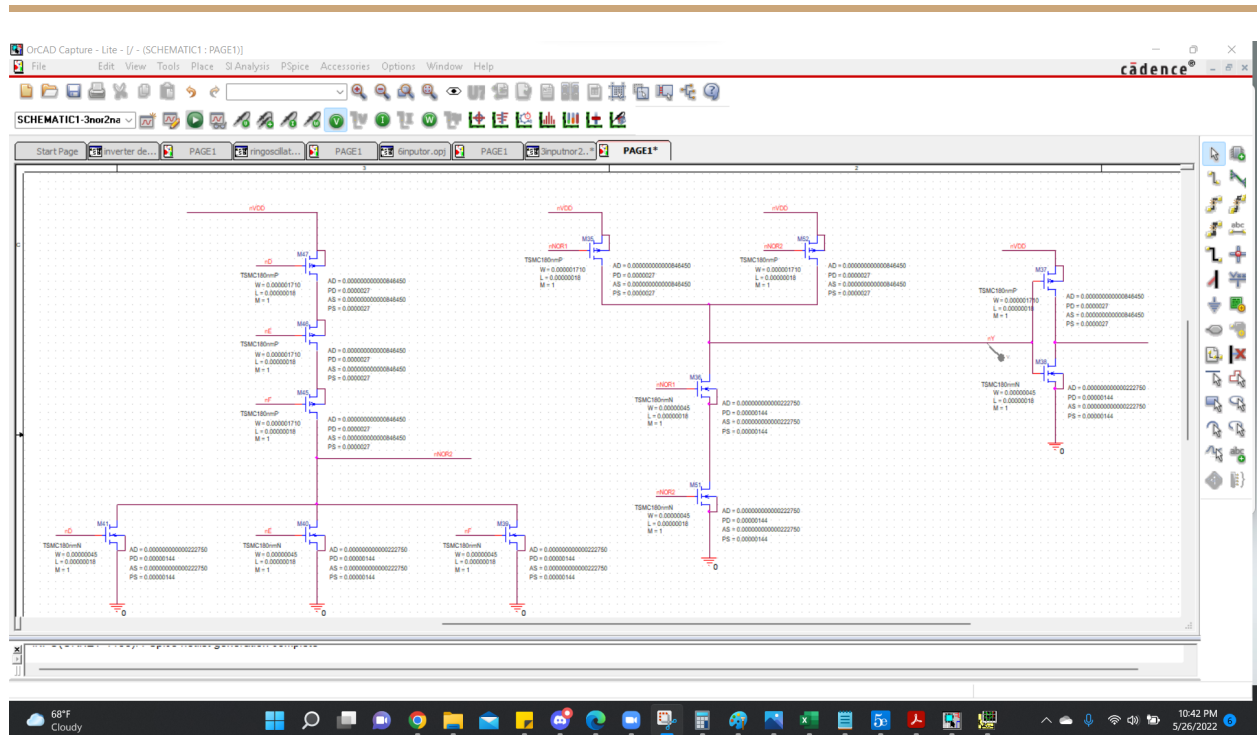

**Figure 3.1.5** 3 input NOR circuit with 2 input NAND circuit schematic for 6 input OR implementation

 

**Figure 3.1.6** 2 x 3 input NOR circuit results, 1 x 2input NAND - 6 input OR implementation results

 

**Figure 3.1.7** 2 x 3 input NOR, 1 x 2 input NAND - 6 input OR circuit simulation to measure delays.

Parameter	6 input OR	2 x 3 input NOR, 1 x 2 input NAND - 6 input OR
$t_r (t_{TLH})$	81.15ps	80.28ps
$t_f (t_{THL})$	137.32ps	140.14ps
$t_{PHL}$	135.76ps	107.95ps
$t_{PLH}$	79.01ps	68.76ps
$t_p$	107.39ps	88.35ps

**Table 3.1.1** 6 input OR gate implementation measurements

---

## Discussion

When we compare the value we designed for the  $V_M$  on the VTC with the values obtained from the simulation we find that they match up to two significant digits. As we did an iterative design process changing the parameters to meet the design requirements, we were able to get the  $V_M$  at the  $V_{DD}/2$  specification. The power peak is basically at  $V_M$ , which we expected as it is the point of transference between the two transistors.

On the ring oscillator, we have the period  $T$  that is almost 10 times  $t_p$ . This makes sense as we have 5 stages and for each period we need 2 delays, one when the signal goes from low to high and another when the signal goes high to low. Each inverter will take on average  $t_p$  to provide output according to an input change and then propagate it to the next inverter on the ring. When we build a ring oscillator using discrete MOS transistors we got different results in terms of scale. This is due to the differences in construction between the discrete and integrated circuit components, which give them different “physical” properties and thus different behavior. For instance,  $V_{DD}$  for the integrated circuit version is just 1.8 V whereas the minimum  $V_{DD}$  for the discrete component is 3V. It takes more time to charge the innate capacitors to a higher voltage, so this also contributes to the higher results for the actual circuit as compared to the simulated ones. The period  $T$  is just 7.5 times  $t_p$ . And the measured  $t_p$  is around 31 times the time specified on the datasheet. This might be due to the capacitance introduced by the connecting cables, connectors, power source, and measuring equipment.

For the CMOS digital designs, we did and simulated we found that the three gate implementation is somewhat faster than the one gate implementation. When we examine the critical paths that signal A has to go through in both cases, we found that the three gate implementation passes that signal through 5 transistors in series whereas the one gate implementation needed one more transistor to do the job. That extra transistor likely causes the extra delay that the one gate implementation shows.



---

## Conclusion

The difference in parameters for discrete MOS devices and integrated circuit devices make them behave at different scales on voltages and speed. The integrated circuit versions work at lower voltages and have a faster response to signal changes. As we design for integrated circuits, compromises between the size of the devices to match properties between the complementary MOSFETS define the final behavior of the devices. Using these characteristics to resemble as close as possible an ideal inverter and using these in the design of more complex CMOS digital logic circuits allows us to get predictable results out of our designs. Designing CMOS digital gates, we see that sometimes a straight-up implementation just bringing up the fan-in of the circuit might not be the fastest implementation. By using multiple gates to chive the same logical operation, we might get a faster implementation by reducing the number of transistors in series that a signal has to pass through to affect a change in an output signal.